

# Architecture: von Neumann; logic gates

---

COSC 208, Introduction to Computer Systems, 2021-10-04

## Outline


- Warm-up
- von Neumann Architecture
- Hardware building blocks
- Logic gates

## Warm-up

*Fill-in the truth tables for all six types of gates*

A	B	A AND B	A OR B	NOT A	A NAND B	A NOR B	A XOR B
0	0	0	0	1	1	1	0
0	1	0	1	1	1	0	1
1	0	0	1	0	1	0	1
1	1	1	1	0	0	0	0

## von Neumann Architecture

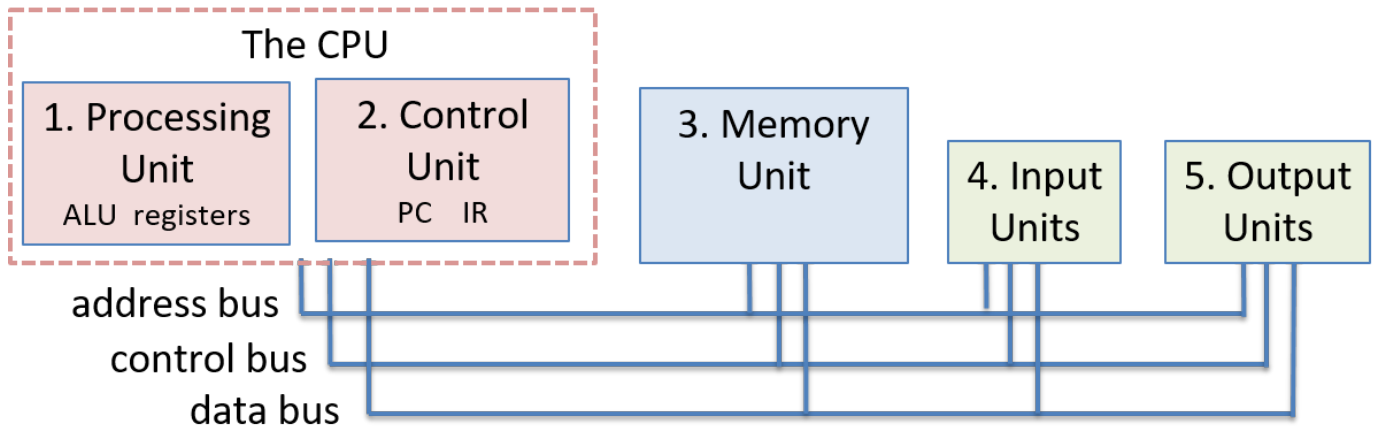


- *Where are instructions stored prior to execution?* — memory unit
- *Where are instructions stored during execution?* — instruction register
- *Where is data stored when it is not in use?* — memory unit
- *Where is data stored when it is being operated on?* — (general purpose) registers
- Notice: instructions and data are both stored in the memory unit, but there are different registers for instructions and data in the CPU
- Fetch-Decode-Execute-Store cycle
  - *What happens in the fetch stage?* — The control unit loads the next instruction from memory, based on the program counter, into the instruction register
  - *What happens in the decode stage?* — break instruction into operation and operands; load operands from memory into registers, if necessary
  - *What happens in the execute stage?* — The ALU performs the operation on the operands
  - *What happens in the store stage?* — The control unit stores the result in memory
- *How can we make this cycle faster?*
  - Pipelining
  - Parallelism
  - Faster bus
  - Faster ALU/control unit
  - Faster memory
  - Use separate memory units for storing instructions and data and separate buses for loading/storing instructions and data; known as the Harvard Architecture, which addresses the von Neumann bottleneck

## Hardware building blocks

- Transistors — switches that control electrical flow; output state depends on current state plus input state
- Logic gates — created from transistors; implement boolean operations (AND, NO, NOT, etc.)
- Circuit — created from logic gates
- Processing, control, and units — created from circuits
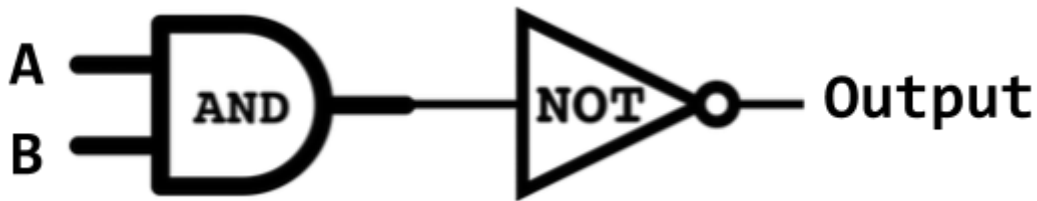
## Building logic gates

- A chip is easier to build if it contains fewer types of gates
- Q4: How do you use AND and NOT gates to create a NAND gate?




- Q5: How do you use OR and NOT gates to create a NOR gate?



- Q6: How do you use NAND gates to create a NOT gate?



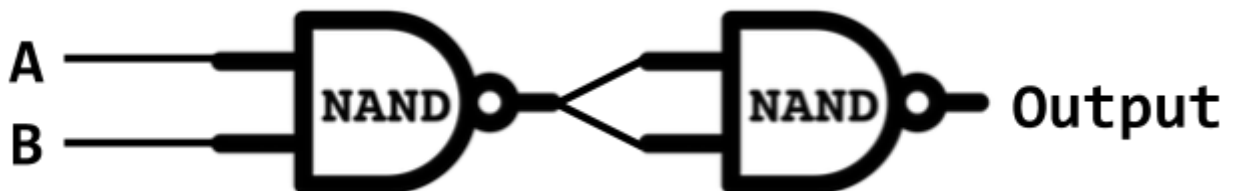- Q7: How do you use NAND gates to create an AND gate?




## 1-bit circuits

- Connect logic gates to perform a more complex operation
- Design the truth table: e.g.,  $A \neq B$

A	B	$A \neq B$
0	0	0
0	1	1
1	0	1
1	1	0

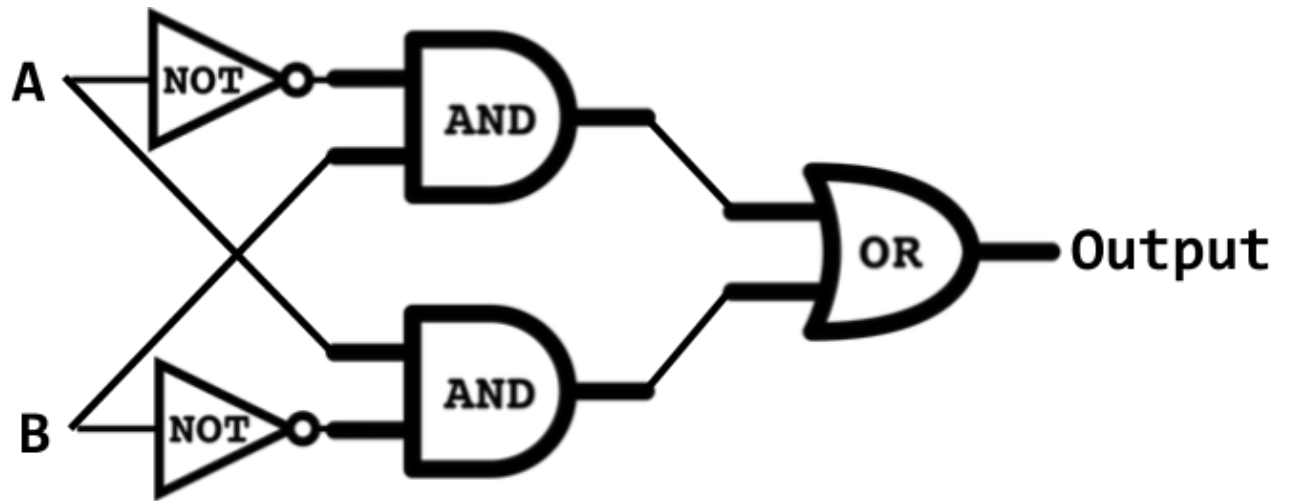- For each row where the output value is 1:
  - Determine how to make each input 1 — e.g., either A or NOT(A)
  - Conjoin the two subexpressions — e.g., NOT(A) AND B
- Create the disjunction of the expressions for each row — e.g., (NOT(A) AND B) OR (A AND NOT(B))
- Create a circuit from left to right, starting with the inner-most subexpressions



- Can we build a circuit that uses fewer gates?

- $A \text{ XOR } B$
- $(A \text{ OR } B) \text{ AND } (\text{NOT } (A \text{ AND } B))$

