

Architecture: von Neumann

COSC 208, Introduction to Computer Systems, 2022-03-08

Outline

- Warm-up
- von Neumann Architecture
- Hardware building blocks

Warm-up

- Assume you are given the following code:

```
struct account {  
    int number; // Account number  
    int balance; // Current account balance  
};  
struct account *open_account(int starting);  
int close_account(struct account *acct);
```


- Q1: Write the *open_account* function, which creates a new account with a random account number and the specified *starting* balance.

```
struct account *open_account(int starting) {  
    struct account *new = malloc(sizeof(struct account));  
    new->number = rand();  
    new->balance = starting;  
    return new;  
}
```

- Q2: Write the *close_account* function, which eliminates the account *acct* and returns the remaining balance.

```
int close_account(struct account *acct) {  
    int remain = acct->balance;  
    free(acct);  
    return remain;  
}
```

von Neumann Architecture

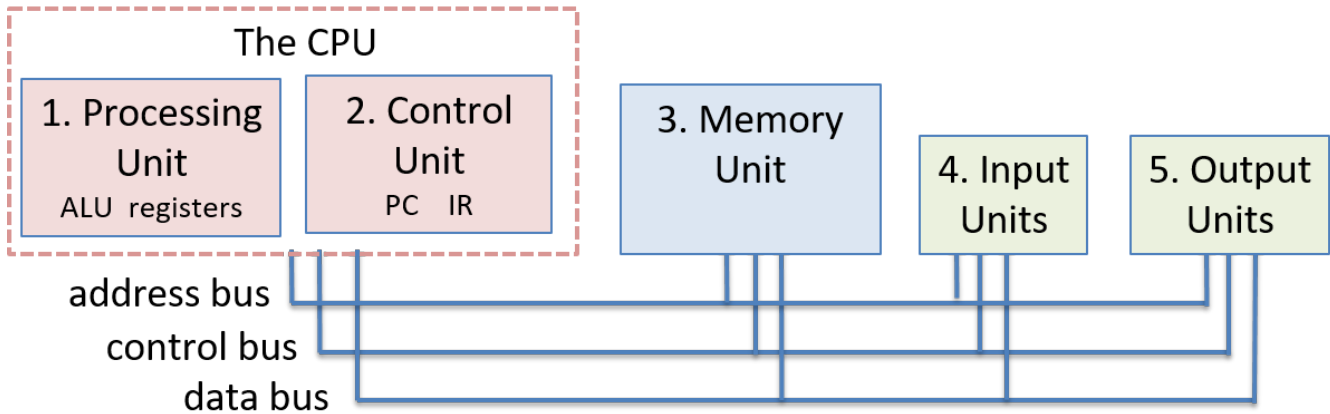

- Where are instructions stored prior to execution? — memory unit
- Where are instructions stored during execution? — instruction register
- Where is data stored when it is not in use? — memory unit
- Where is data stored when it is being operated on? — (general purpose) registers
- Notice: instructions and data are both stored in the memory unit, but there are different registers for instructions and data in the CPU
- Fetch-Decode-Execute-Store cycle
 - What happens in the fetch stage? — The control unit loads the next instruction from memory, based on the program counter, into the instruction register
 - What happens in the decode stage? — break instruction into operation and operands; load operands from memory into registers, if necessary
 - What happens in the execute stage? — The ALU performs the operation on the operands
 - What happens in the store stage? — The control unit stores the result in memory
- How can we make this cycle faster?
 - Pipelining
 - Parallelism
 - Faster bus
 - Faster ALU/control unit
 - Faster memory
 - Use separate memory units for storing instructions and data and separate buses for loading/storing instructions and data; known as the Harvard Architecture, which addresses the von Neumann bottleneck

Hardware building blocks

- Transistors — switches that control electrical flow; output state depends on current state plus input state
- Logic gates — created from transistors; implement boolean operations (AND, OR, NOT, etc.)
- Circuit — created from logic gates
- Processing, control, and units — created from circuits

Fill-in the truth tables for all six types of gates

A	B	A AND B	A OR B	NOT A	A NAND B	A NOR B	A XOR B
0	0	0	0	1	1	1	0
0	1	0	1	1	1	0	1
1	0	0	1	0	1	0	1
1	1	1	1	0	0	0	0

Building logic gates

- A chip is easier to build if it contains fewer types of gates
- Q4: How do you use AND and NOT gates to create a NAND gate?



- Q5: How do you use OR and NOT gates to create a NOR gate?



- Q6: How do you use NAND gates to create a NOT gate?



- Q7: How do you use NAND gates to create an AND gate?

